

assignment 11

solution to gate EC 2014-2, question 9

dilip

IIIT RAICHUR

January 2021



Table of Contents

1 Question

2 Answer

- Master-Slave D flip flop
- Transition Table
- State Diagram



Question Figure

 


Figure: Question Diagram



Question Text

Current option is

- (a) JK flip-flop
- (b) SR flip-flop
- (c) D flip-flop
- (d) Master-slave arrangement



Table of Contents

1 Question

2 Answer

- Master-Slave D flip flop
- Transition Table
- State Diagram



The correct option is d) Master-slave arrangement.



The basic D-type flip flop can be improved further by adding a second SR flip flop to its output that is activated on the complementary clock signal to produce a "Master-Slave D-type flip flop". On the leading edge of the clock signal (LOW-to-HIGH) the first stage, the "master" latches the input condition at D, while the output stage is deactivated.

On the trailing edge of the clock signal (HIGH-to-LOW), the second "slave" stage is now activated, latching on to the output from the first master circuit. Then the output stage appears to be triggered on the negative edge of the clock pulse. "Master-Slave D-type flip flop" can be constructed by the cascading together of two latches with opposite clock phases as shown.



Transition Table

Present State		Input	Next state		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0



State Diagram

 


Figure: State Diagram



Timing Diagrams

 


Figure: Timing diagram

